

Your Lab Problem


1. Plot graph of $|Z_C|$, $|Z_L|$, $|Z_T|$, $|v_R|$, $|v_C|$, $|v_L|$, $|i|$ versus ω (from 10 – 10,000 rad/sec).
2. Find the frequency, ω , at which the current, $|i|$, is maximum. Use the “log scale” on frequency axis.

$$v_s = 12 \cos(\omega t) \text{V},$$

$$R = 100\Omega,$$

$$C = 40\mu\text{F},$$

$$L = 100\text{mH}$$

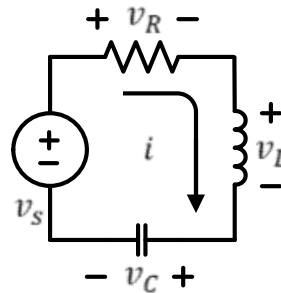

16

Your work

Find your own work that can be applied by MATLAB.

1. Clearly Explain what you want to do.
2. Step-by-Step show how to calculate the output.
3. Show MATLAB code with the comments
4. Present your result(s) in graphs and/or numbers.
5. Conclude how MATLAB can help you do this work.

17